

EE 214: Digital Circuits Lab

Homework-1 Submission

Roll No. 200070054

Q.1. This zip file contains all the needed files.

Gates.vhdl

add_sub.vhdl

Full_Adder.vhdl

DUT.vhdl

Testbench.vhdl

TRACEFILE.txt

Q.2. Effect of different values of M on the functionality of a given circuit:


1. For $M=1$, the circuit behaves like a 4-bit ripple carry subtractor
2. For $M=0$, the circuit behaves like a 4-bit ripple carry adder.

Q.3. The simulation folder in this zip file contains the output file generated after RTL and Gate Level Simulation.

Explanation of part-B

→ Truth table of a XOR gate,

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 

→ now in our problem we are giving B_0, B_1, B_2 and B_3 with M as a input to XOR gate & its output to full adder with A_0, A_1, A_2 and A_3

$$\text{so } M \oplus B_i = \begin{cases} B_i, & \text{if } M = 0 \\ \bar{B}_i, & \text{if } M = 1 \end{cases}$$

⇒ so the input to full adder will be
 A_i & B_i when $M = 0$
& A_i & \bar{B}_i when $M = 1$

⇒ so this circuit will add A_i & B_i for $M = 0$ & subtract for $M = 1$.

→ conclusion: This four bit ripple carry adder will behave like a subtractor when $M = 1$ & a adder when $M = 0$.