

Combinational Circuit 1

Wadhvani Electronics Lab, IIT Bombay

Thursday 11th August, 2021


[\[Download this handout as PDF\]](#)

Use structural modelling for this experiment; means instantiate components and use port map to connect those components

Part-A: 2 to 4 decoder

 (i) Design [3 Marks]

Design a 2 to 4 decoder with enable input as shown in figure below. Use only 2 or 3 input AND / NAND gate and inverters. (Assume enable as active high input)



! INFO

Decoders are combinational circuit which takes in binary information in the form of N input lines and change the binary information into 2^N output lines.

Hint: See Tracefile to understand the functionality of decoder

(ii) VHDL description [5 Marks]

Describe a 2 to 4 decoder with enable input in VHDL.

(iii) Simulation [5 Marks]

Simulate the decoder using the generic testbench to confirm the correctness of your description.

i NOTE

To do this, you need to use the given tracefile and modify the testbench given to you appropriately.

Tracefile format <A1 A0> <E> <Y3 Y2 Y1 Y0> 1111 [Tracefile](#)

Part-B: 3 to 8 decoder

(i) Design [3 Marks]

Design a 3 to 8 decoder with enable input using 2 to 4 decoder designed in part A

! INFO

3 data input
1 enable input
 $2^3 = 8$ output lines

(ii) VHDL description [5 Marks]


Describe a 3 to 8 decoder with enable input in VHDL.

(iii) Simulation [5 Marks]

Simulate the decoder using the generic testbench to confirm the correctness of your description.

i NOTE

To do this, you need to use the given tracefile and modify the testbench given to you appropriately.

Tracefile format<A2 A1 A0> <E> <Y7 Y6 Y5 Y4 Y3 Y2 Y1 Y0> 11111111Tracefile 

Part-C: Full adder using 3 to 8 decoder

(i) Design [3 Marks]

Design full adder using 3 to 8 decoder designed in part B

(ii) VHDL description [5 Marks]

Describe full adder using 3 to 8 decoder in VHDL.

(iii) Simulation [5 Marks]

Simulate this full adder using the generic testbench to confirm the correctness of your description.

i NOTE

To do this, use the given tracefile (from full adder demo resources) and modify the testbench given to you appropriately.

Tracefile format<A B Cin> <S Cout> 11